

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

600-MHz COUNTER

A battery-powered 600-MHz frequency counter that's small enough to fit in the palm of your hand. Build it for less than 17 cents per MHz. Turn to page 39.

VIDEO MOTORCYCLE GAME

Rev your engine, hang a wheelie, accelerate up the ramp and see how many obstacles you can jump. Construction starts on page 44.

DIGITAL CIRCUIT DESIGN


Part 2. How to design digital circuits from scratch. The walk through sequential and combinational circuits and circuit reduction techniques starts on page 47.

4-CHANNEL FM

A look at the different broadcast systems under consideration by the FCC and what it will mean to you. For the complete story, turn to page 51.


PLUS:

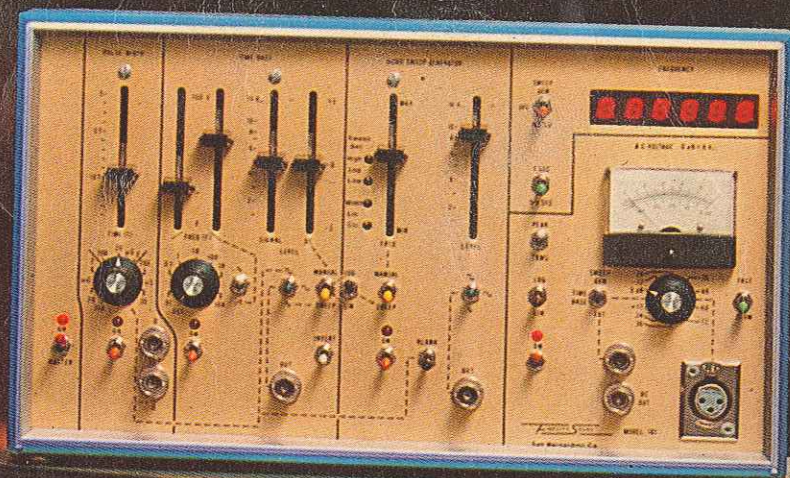- ★ Build a NOM card for an 1802-based computer
- ★ Hobby Corner
- ★ Computer Corner
- ★ Jack Darr's Service Clinic
- ★ 2 Hi-Fi Lab Test Reports



COVER STORY AUDIO TEST STATION

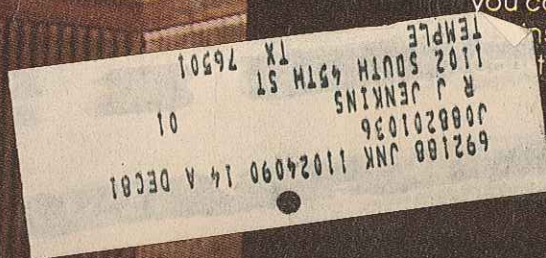Professional-quality test instrument you can build combines several important instruments into a single cabinet. Construction starts on page 35.



NOM Card For The 1802

Part 2—Add-on math board for an 1802-based microcomputer. Based on a number-crunching IC, this board speeds execution time, reduces software overhead and saves memory

L. STEVEN CHEAIRS

LAST MONTH WE LOOKED AT HOW THE NOM card reduces computer memory requirements and increases processing speed by eliminating number-crunching software routines. This month, we present final construction details.

Construction

The components used in this project are all readily available; assembly is straightforward; and the circuit can be wire-wrapped or built on a PC card.

Use a double-sided glass epoxy circuit board with 2-ounce copper foil (available from Questar). A heavy plate layer covers all runs, and the holes are plated-through. The card has gold-plated fingers and a solder mask. For those who wish to etch the circuit board themselves, the foil patterns are shown in Figs. 8 and 9.

In assembling the board, pay special attention to component orientation. Figure 10 shows the correct placement and orientation of all the components and Fig. 11 shows the PC board pinout and switch placement. First, install and solder all resistors, capacitors and diodes. Connect the +5-volt and -15-volt leads, (the -4 volts is derived from the -15-volt source) and methodically test all power-supply pads for the proper voltages. If the power levels are OK, disconnect the power and install the IC's; if not, check for possible shorts or faulty components. No calibration is required.

Check-out and operation

Check-out and operation is theoretically very simple. First, enter the first number into the X-register. Follow this with the next number; all numbers enter the X-register. Execute a math operation,

such as an ADD. Enter and execute an OUT instruction. If the correct answer is obtained, then 90% of the test is complete,

and the only remaining functions to test are error and branch. If you did not receive the correct answer, check to see if

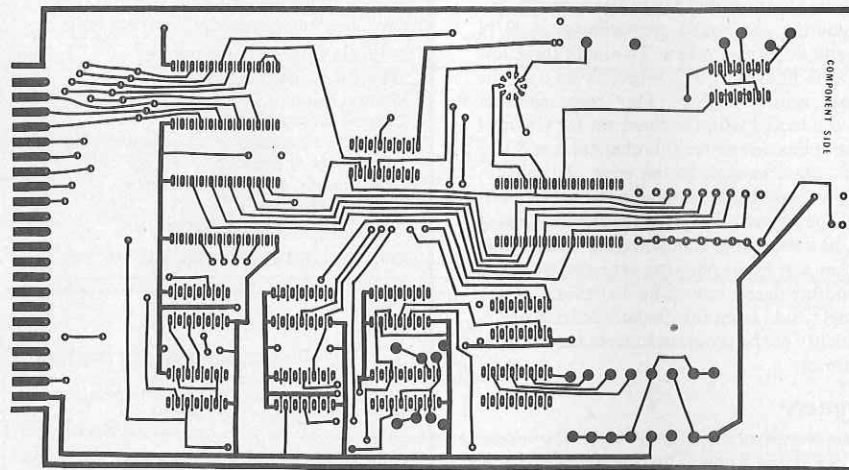


FIG. 8—PRINTED CIRCUIT PATTERN for the component-side of the NOM card.


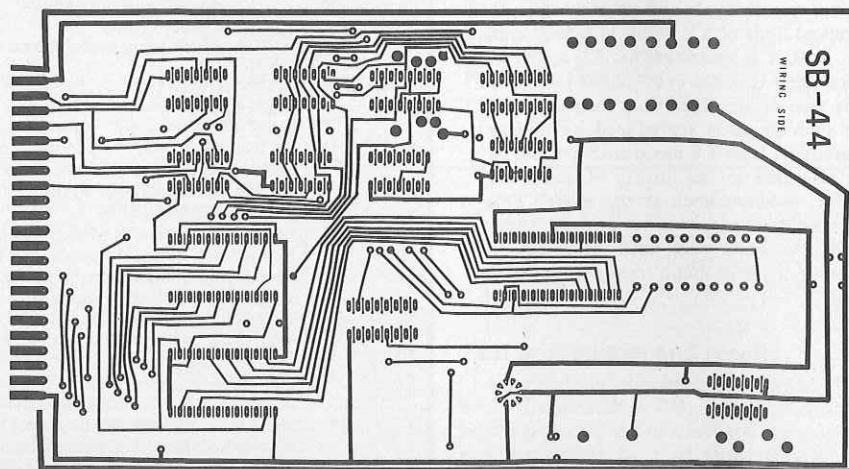


FIG. 9—PRINTED CIRCUIT PATTERN for the foil-side of the NOM card.

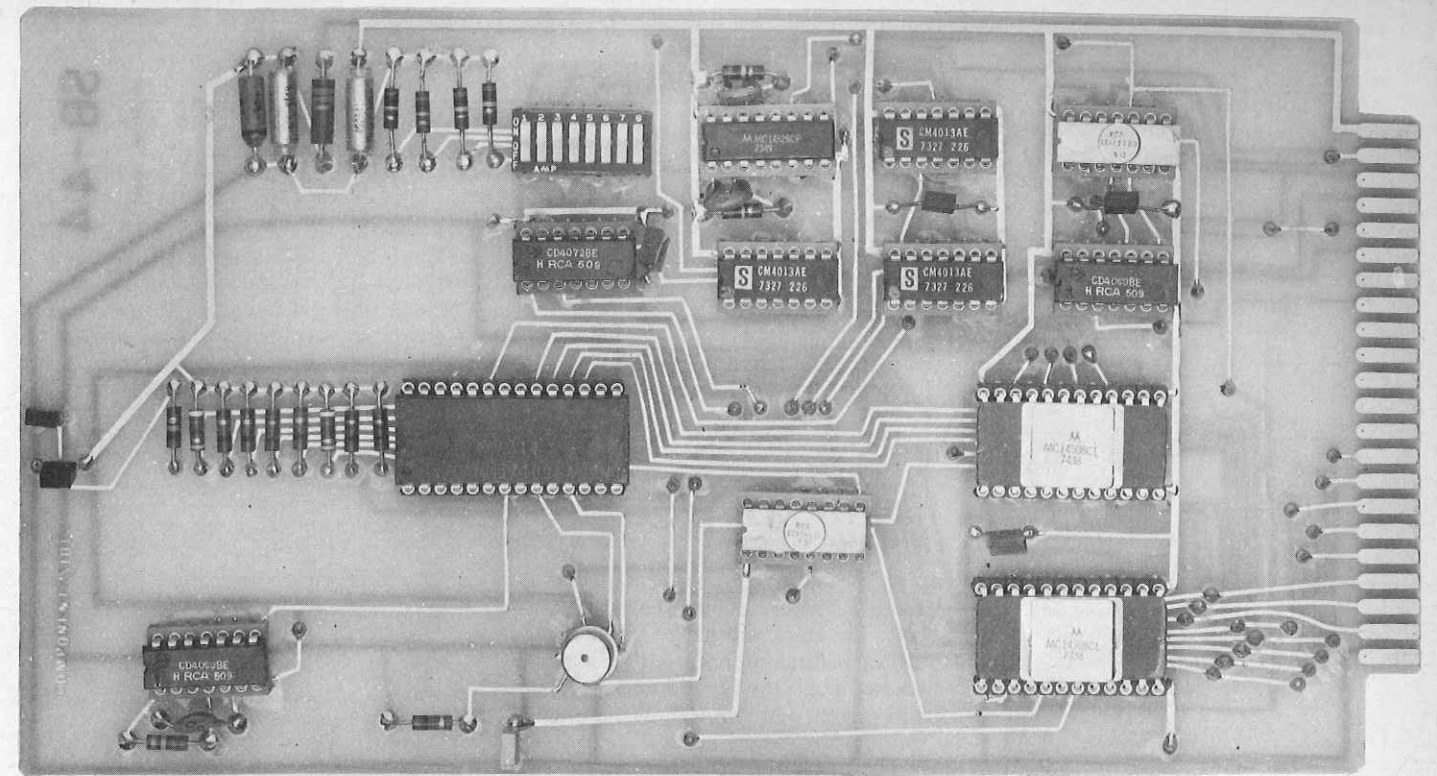

all the DIP switches were closed; if so, then recheck component placement and orientation. If no mistake was made (and you have programmed the 1802 correctly), then a component failure has occurred. Use normal digital troubleshooting techniques to isolate and solve the problem.

Now, enter a branch instruction to see if the branch outline interrupts the 1802. If this works, proceed to the final test. Enter a zero into the X-register, then execute the 1/X instruction. If an error occurs, you have completed the NOM interface; if not, check the error flip-flop.

The basic operation is outlined in the flowchart shown in Fig. 12. The user program first places the numbers in a FIFO table along with the required mathematical operations. Enter the first number into the X-register, then exchange the X- and Y-registers. Now, enter the next number into the X-register, then perform the desired operations. Enter the next number (if any) and perform the desired operations. Continue until all numbers and operations are completed. Execute an OUT instruction, store the digits into the user's FIFO table and return to the user program. The above description implies that the 1802 is tied up 100% of the time with the NOM, but actually a very small percentage of the 1802's time is spent with the NOM during these operations. The 1802 only moves data/instruction into (and out) of the NOM; most of the time it is used to perform mathematical calculations or to manipulate data inside the NOM. During this time the 1802 is free to perform other tasks.

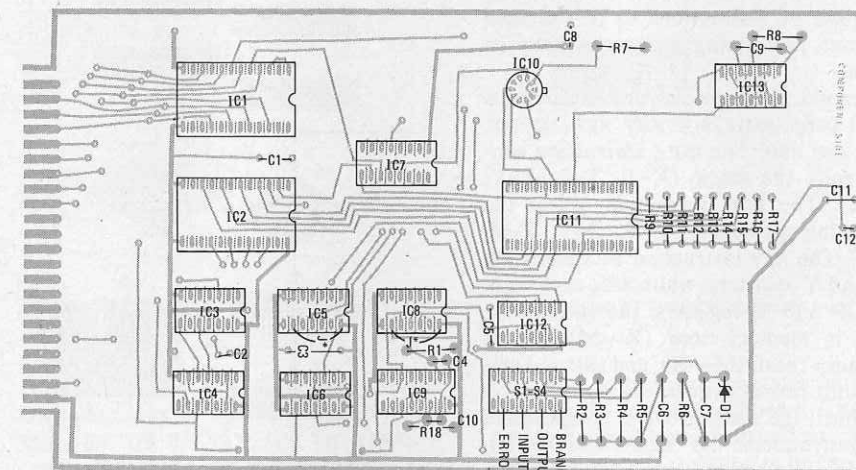


FIG. 10—COMPONENT PLACEMENT DIAGRAM shows where the parts go on the circuit board.

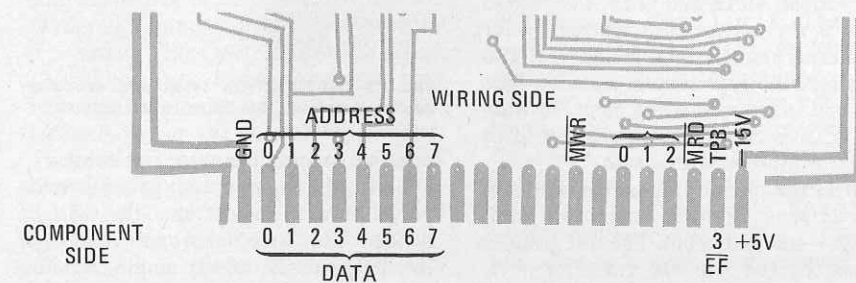


FIG. 11—PINOUT DIAGRAM shows where connections on the circuit board go.

